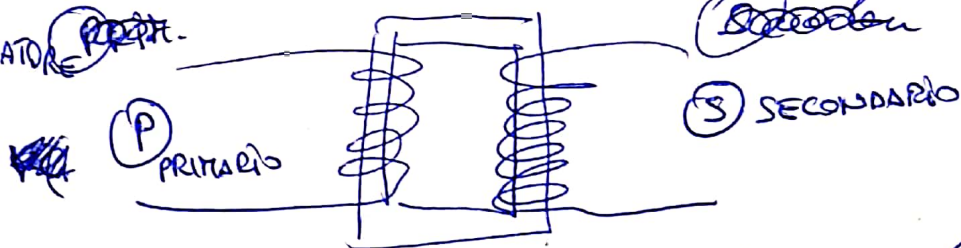


nº 4

TRANSFORMADOR



$$V_p = 220V$$

$$N_p = 300 \text{ arv}$$

$$V_s = 20 \text{ KV}$$

$$N_s = ?$$

A)
$$\frac{N_s}{N_p} = \frac{V_s}{V_p} \rightarrow N_s = N_p \cdot \frac{V_s}{V_p} = 300 \cdot \frac{20.000V}{220V}$$

$$N_s = 27.272$$

B)
$$\hat{i}_p = 0,4 \text{ A}$$

$$\hat{i}_s = ?$$

$$\frac{\hat{i}_s}{\hat{i}_p} = \frac{V_p}{V_s} = \frac{N_p}{N_s}$$

$$\hat{i}_s = \hat{i}_p \frac{V_p}{V_s} = 0,4 \text{ A} \cdot \frac{220V}{20.000V} = 4,4 \cdot 10^{-3} \text{ A}$$